

Analog Android Drum Machine

Vince Coghlan and Zack Vogel
ECEN3000


April 30, 2014

1 Introduction


Analog drum machines are used by many modern musicians as a matter of convenience, and that is indeed why they were initially created. After many years of musical development, however, the sounds of a real analog drum machine are now associated with artists like Kanye West, Todd Terje, Can, and Marvin Gaye. With modern technology, any normal person can take a great photograph, or make a good movie. Smartphones and miniature CCD technology have allowed for the typical consumer to become an artist, expressing their creativity with very little talent. This is, however, not the case with music. One needs to spend months learning the guitar, playing drums, annoying the neighbors, and hurting fingers to create anything that is even somewhat pleasant. With a drum machine, a regular person can become an artist. With a few button clicks, it will do exactly what you want with perfect tempo. Modern drum machines like the famous TR-808 [1] and Oberheim DMX [2] cost upwards of \$1000. This is due to the high quality components, the difficulty of design and manufacture, and the vast array of features. We wanted to make a drum machine that could be used from a cell phone, and that only costs a few dollars.

2 Background

An analog drum machine is a seemingly complicated set of circuits that, through the magic of electronics, is surprisingly simple. A drum sound is really just a decaying sine wave at a specific frequency. For a bass drum that frequency might be 20–50Hz, for a high tom, that might be 150+Hz. To achieve this, a short pulse is sent into an op-amp, which then oscillates as it slowly decays. This sounds quite realistic, but it doesn't have to. We want to achieve the classic analog drum sound, not a real drum design. The oscillator circuit for the bass drum looks like so:

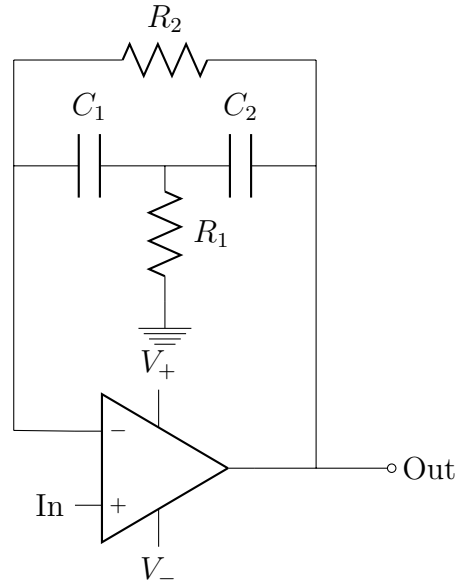

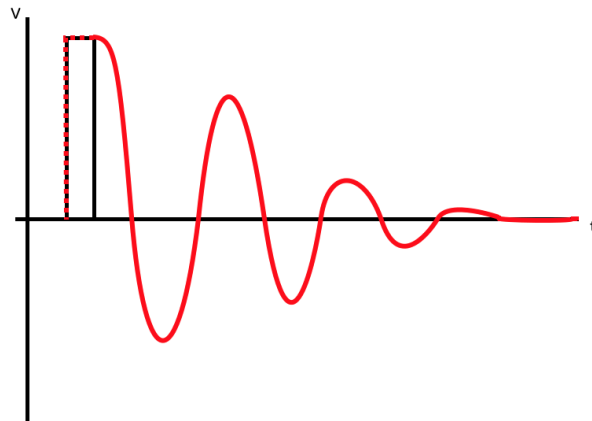This circuit, when given a pulse, will respond like so:




Some circuit analysis will tell us that the frequency and quality is

$$f = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}} \quad Q = \frac{\sqrt{\frac{R_2}{R_1}}}{\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}}}$$

These equations and the circuit are given in [1]. Changing any of these values will effect the frequency response and the decay of the circuit. These values aer quite difficult to get just right, the TR-808 implements R_2 as a large potentiometer so that you can change the tune of the drum. A snare drum is a combination of two sounds. The sound of the drum, and the sound of the snare. This can be accomplished quite well by triggering the same drum

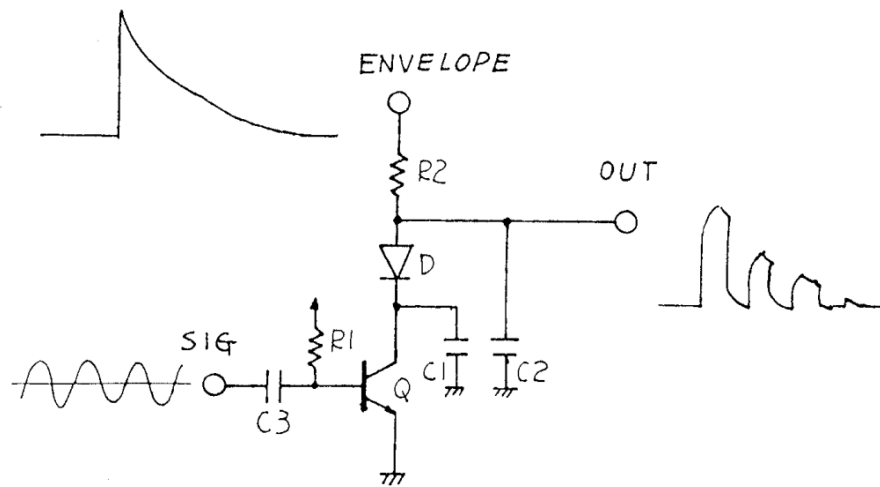circuit as above with a decaying pulse of white noise. The circuit for the white noise was also given in the schematics for the TR-808 [1]:



The white noise was generated by a Linear Feedback Shift Register [3]. Additionally, our cymbal circuit is just a decaying burst of the white noise.

All of these various instruments are then mixed in an op-amp and outputted in a two line interface to be fed into an amplifier.

References

- [1] Roland Corporation, “TR-808 Service Manual”, <http://ericarcher.net/wp-content/uploads/2009/11/808-svc-man.pdf>, 1983.
- [2] Oberheim Electronics, “Oberheim DMX Schematics” <http://www.electrongate.com/obfiles/index.html>, 1981.
- [3] C. Stroud, “Linear Feedback Shift Registers”, Dept. of ECE, Auburn, <http://www.eng.auburn.edu/~strouce/class/elec6250/LFSRs.pdf>, 2004